

ENGR& 204 Homework 6 extra problem

A laser pulse power circuit is shown in the figure below. It is required that $v(0) = 7.0$ v and $i(0) = 3.8$ A. Find the R , the resistance required for these conditions. Assume that the switch has been closed for a long time before it is opened at $t = 0$.

