

1. A digital multimeter (DMM) is connected to a resistor circuit as shown. If the resistance of the DMM is $1\text{ M}\Omega$, what value will be displayed if the DMM is measuring resistance as shown?

