

## ENGR& 204 Spring 2010 Homework 5 Key

The voltage at the terminals of the  $300 \mu\text{H}$  inductor is shown. The current  $i$  is zero for  $t \leq 0$ . Find an equation for  $i$  for  $t \geq 0$ , Sketch  $i$  vs  $t$  for  $0 \leq t \leq \infty$ .

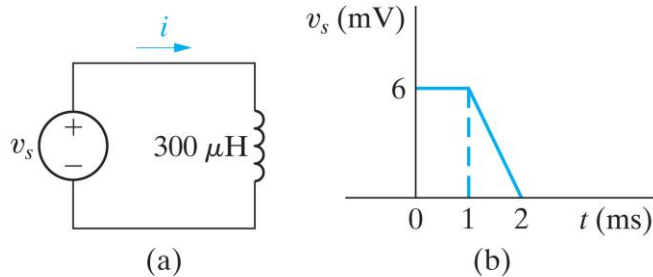


Figure: 06-36-011a,bP6.02  
Copyright © 2008 Pearson Prentice Hall, Inc.

P 6.2 [a]  $0 \leq t \leq 1 \text{ ms}$  :

$$i = \frac{1}{L} \int_0^t v_s dx + i(0) = \frac{10^6}{300} \int_0^t 6 \times 10^{-3} dx + 0$$

$$= 20x \Big|_0^t = 20t \text{ A}$$

$1 \text{ ms} \leq t \leq 2 \text{ ms}$  :


$$i = \frac{10^6}{300} \int_{10^{-3}}^t (12 \times 10^{-3} - 6x) dx + 20 \times 10^{-3}$$

$$\therefore i = 40t - 10,000t^2 - 10 \times 10^{-3} \text{ A}$$

$2 \text{ ms} \leq t \leq \infty$  :

$$i = \frac{10^6}{300} \int_{2 \times 10^{-3}}^t (0) dx + 30 \times 10^{-3} = 30 \text{ mA}$$

[b]

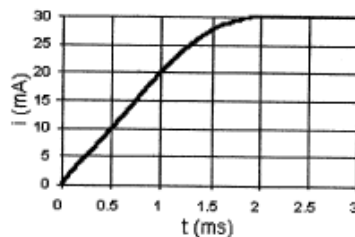

6.8 The current in a  $15 \text{ mH}$  inductor is  $1 \text{ A}$  for  $t \leq 0$  and given by  $i = A_1 e^{-2000t} + A_2 e^{-8000t} \text{ A}$  for  $t \geq 0$ . The voltage across the inductor is  $60 \text{ V}$  at  $t = 0$ . Find the voltage across the inductor for  $t > 0$ , and find the time when the power at the terminals of the inductor is zero.

P 6.8 [a]  $i(0) = A_1 + A_2 = 1$

$$\frac{di}{dt} = -2000A_1e^{-2000t} - 8000A_2e^{-8000t}$$

$$v = -30A_1e^{-2000t} - 120A_2e^{-8000t} \text{ V}$$

$$v(0) = -30A_1 - 120A_2 = 60$$

Solving,  $A_1 = 2$  and  $A_2 = -1$

Thus,

$$i_1 = (2e^{-2000t} - e^{-8000t}) \text{ A} \quad t \geq 0$$

$$v = -60e^{-2000t} + 120e^{-8000t} \text{ V}, \quad t \geq 0$$

[b]  $p = vi = 300e^{-10,000t} - 120e^{-4000t} - 120e^{-16,000t}$

$$p = 0 \quad \text{when} \quad 300e^{6000t} - 120e^{12,000t} - 120 = 0$$

$$\text{Let } x = e^{6000t}; \quad \text{then} \quad 300x - 120x^2 - 120 = 0$$

$$\text{Thus } x^2 - 2.5x + 1 = 0 \quad \text{so} \quad x = 0.5 \text{ and } x = 2$$

If  $x = e^{6000t} = 0.5$ ,  $t$  will be negative. Hence, the solution for  $t > 0$  must be  $x = 2$ :

$$e^{6000t} = 2 \quad \text{so} \quad 6000t = \ln 2$$

$$\text{Thus, } t = \frac{\ln 2}{6000} = 115.52 \mu\text{s}$$

6.17 The current shown is applied to a  $0.25 \mu\text{F}$  capacitor with zero initial volts. Find the charge at  $t = 30 \mu\text{s}$ , voltage at  $t = 50 \mu\text{s}$ , and energy stored in the capacitor by this current.

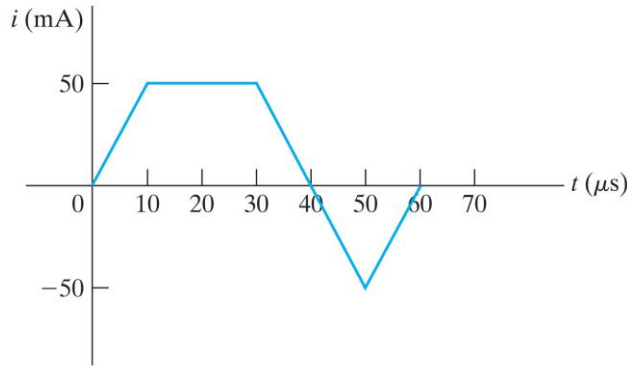


Figure: 06-36-08P6.17  
Copyright © 2008 Pearson Prentice Hall, Inc.

$$\text{P 6.17 [a]} \quad i = \frac{50 \times 10^{-3}}{10 \times 10^{-6}} t = 5 \times 10^3 t \quad 0 \leq t \leq 10 \mu\text{s}$$

$$i = 50 \times 10^{-3} \quad 10 \leq t \leq 30 \mu\text{s}$$

$$\begin{aligned} q &= \int_0^{10 \times 10^{-6}} 5 \times 10^3 t \, dt + \int_{10 \times 10^{-6}}^{30 \times 10^{-6}} 50 \times 10^{-3} \, dt \\ &= 5 \times 10^3 \frac{t^2}{2} \Big|_0^{10 \times 10^{-6}} + 50 \times 10^{-3} (20 \times 10^{-6}) \\ &= 5 \times 10^3 \left(\frac{1}{2}\right) (100 \times 10^{-12}) + 1000 \times 10^{-3} \times 10^{-6} \\ &= 1.25 \mu\text{C} \end{aligned}$$

$$\text{[b]} \quad i = 200 \times 10^{-3} - 5 \times 10^{-3} t \quad 30 \mu\text{s} \leq t \leq 50 \mu\text{s}$$

$$\begin{aligned} q &= 1.25 \times 10^{-6} + \int_{30 \times 10^{-6}}^{50 \times 10^{-6}} [200 \times 10^{-3} - 5 \times 10^3 t] \, dt \\ &= 1.25 \times 10^{-6} + 200 \times 10^{-3} (20 \times 10^{-6}) - 5 \times 10^3 \frac{t^2}{2} \Big|_{30 \times 10^{-6}}^{50 \times 10^{-6}} \\ &= 1.25 \times 10^{-6} + 4000 \times 10^{-9} - 5 \times 10^3 \left[ \frac{2500 - 900}{2} \right] 10^{-12} \\ &= 1.25 \mu\text{C} \end{aligned}$$

$$\text{Since } q = vC, \quad \therefore v = 1.25/0.25 = 5 \text{ V.}$$

$$\text{[c]} \quad i = -300 \times 10^{-3} + 5 \times 10^{-3} t \quad 50 \mu\text{s} \leq t \leq 60 \mu\text{s}$$

$$\begin{aligned} q &= 1.25 \times 10^{-6} + \int_{50 \times 10^{-6}}^{60 \times 10^{-6}} [-300 \times 10^{-3} + 5 \times 10^3 t] \, dt \\ &= 1.25 \times 10^{-6} - 300 \times 10^{-3} (10 \times 10^{-6}) \\ &\quad + 5 \times 10^3 \left[ \frac{3600 - 2500}{2} \right] 10^{-12} \\ &= 1 \mu\text{C} \end{aligned}$$

$$v = \frac{1 \times 10^{-6}}{0.25 \times 10^{-6}} = 4 \text{ V}$$

$$w = \frac{C}{2} v^2 = \frac{1}{2} (0.25) \times 10^{-6} (16) = 2 \mu\text{J}$$

6.23 The voltage  $v_o = 1250e^{-25t}$  V. If  $i_1(0) = 10$  A and  $i_2(0) = -5$  A, find  $i_o(0)$ ,  $i_o(t)$  for  $t \geq 0$ ,  $i_1(t)$  for  $t \geq 0$ ,  $i_2(t)$  for  $t \geq 0$ , the initial energy stored in the three inductors, the total energy delivered to the black box, and the energy trapped in the ideal inductors.


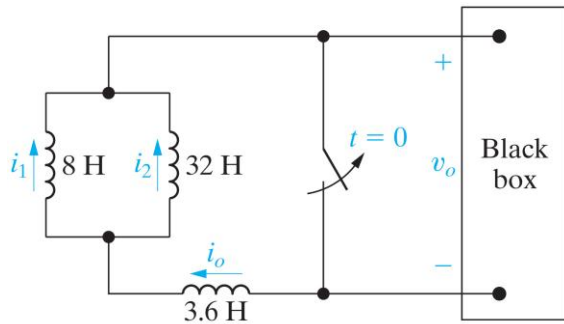


Figure: 06-36-14P6.23  
Copyright © 2008 Pearson Prentice Hall, Inc.

P 6.23 [a]  $i_o(0) = i_1(0) + i_2(0) = 5 \text{ A}$


[b]

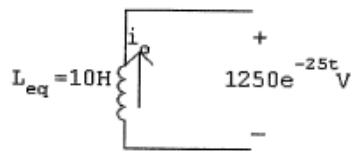

$$i_o = -\frac{1}{10} \int_0^t 1250e^{-25x} dx + 5 = -125 \left[ \frac{e^{-25x}}{-25} \right]_0^t + 5$$

$$= 5(e^{-25t} - 1) + 5 = 5e^{-25t} \text{ A}, \quad t \geq 0$$

[c]

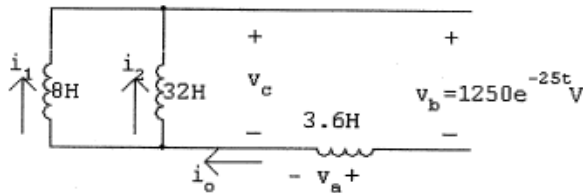

$$v_a = 3.6 \frac{d}{dt}(5e^{-25t}) = -450e^{-25t} \text{ V}$$

$$v_c = v_a + v_b = -450e^{-25t} + 1250e^{-25t}$$

$$= 800e^{-25t} \text{ V}$$

$$i_1 = -\frac{1}{8} \int_0^t 800e^{-25x} dx + 10$$

$$= 4e^{-25t} - 4 + 10$$

$$i_1 = 4e^{-25t} + 6 \text{ A} \quad t \geq 0$$

[d]  $i_2 = -\frac{1}{32} \int_0^t 800e^{-25x} dx - 5$

$$= e^{-25t} - 1 - 5$$

$$i_2 = e^{-25t} - 6 \text{ A}, \quad t \geq 0$$

[e]  $w(0) = \frac{1}{2}(8)(100) + \frac{1}{2}(32)(25) + \frac{1}{2}(3.6)(25) = 845 \text{ J}$

[f]  $w_{\text{del}} = \frac{1}{2}(10)(25) = 125 \text{ J}$

[g]  $w_{\text{trapped}} = 845 - 125 = 720 \text{ J}$

7.8 The switch has been closed a long time. At  $t = 0$  it is opened. Find  $v_o(t)$  for  $t \geq 0$ .


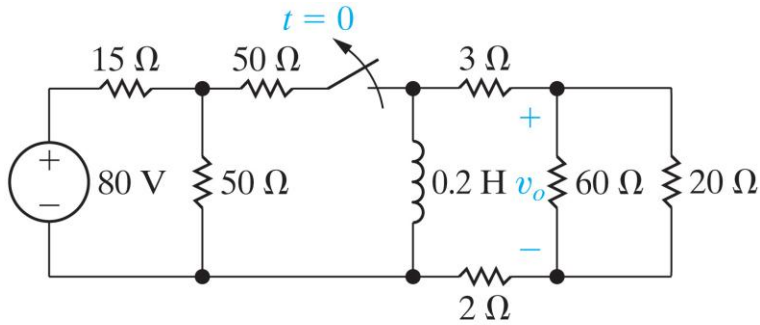


Figure: 07-48-07P7.08

Copyright © 2008 Pearson Prentice Hall, Inc.

P 7.8 [a] For  $t < 0$


Note: use the cookbook!

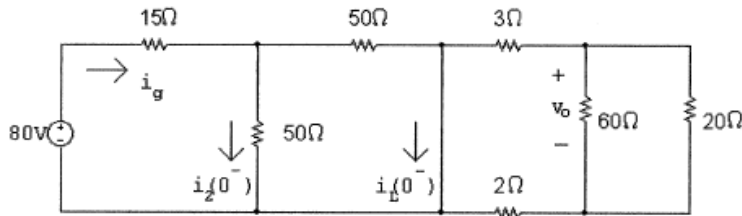

$$i_g = \frac{80}{40} = 2 \text{ A}$$

$$i_L(0^-) = \frac{2(50)}{(100)} = 1 \text{ A} = i_L(0^+)$$

For  $t > 0$

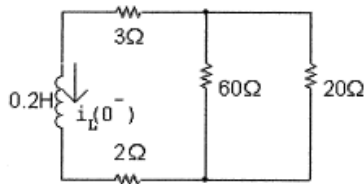

$$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{0.20}{5 + 15} = \frac{1}{100} = 0.01 \text{ s}$$

$$i_L(0^+) = 1 \text{ A}$$

$$i_L(t) = e^{-100t} \text{ A}, \quad t \geq 0$$

$$v_o(t) = -15i_L(t)$$

$$v_o(t) = -15e^{-100t} \text{ V}, \quad t \geq 0^+$$

7.14 The switch has been closed a long time and opens at  $t = 0$ . Find  $v_o(t)$  for  $t \geq 0^+$


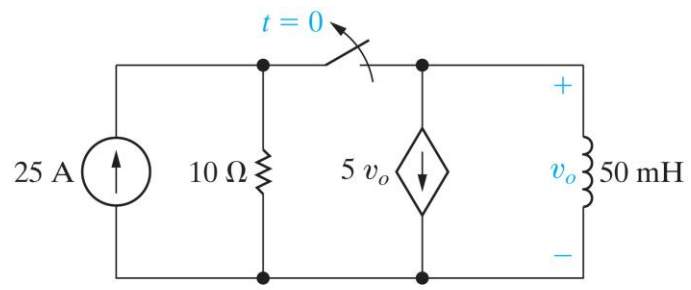


Figure: 07-48-11P7.14  
Copyright © 2008 Pearson Prentice Hall, Inc.


P 7.14  $t < 0$

Note: use the cookbook!

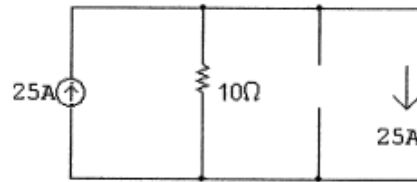


$$i_L(0^-) = i_L(0^+) = 25 \text{ A}$$

$t > 0$

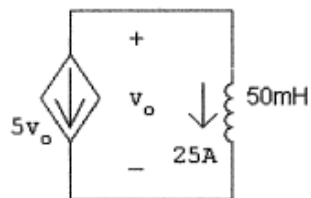


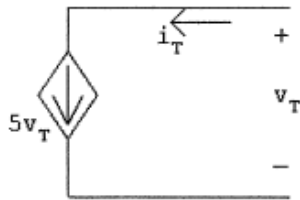Find Thévenin resistance seen by inductor



$$i_T = 5v_T; \quad \frac{v_T}{i_T} = R_{Th} = \frac{1}{5} = 0.2 \Omega$$
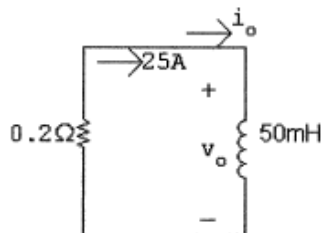
$$\tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{0.2} = 250 \text{ ms}; \quad 1/\tau = 4$$



$$i_o = 25e^{-4t} \text{ A}, \quad t \geq 0$$

$$v_o = L \frac{di_o}{dt} = (50 \times 10^{-3})(-100e^{-4t}) = -5e^{-4t} \text{ V}, \quad t \geq 0^+$$