

ENGR 204 Spring 2011 Test 1 Name: Key

You can use Orcad Pspice to check problems 1 - 5 only. But for #6 you must use the program.


- 1) For the circuit shown,  $i(t) = 2t$  amps and  $v(t) = 3t^2$  volts. A) Find the power at 1.0 s and say whether the device is supplying or absorbing power. B) Find the total energy the device supplies or absorbs from  $t = 0$  to  $t = 1.0$  s.

$$A) P = -V\dot{i}$$

$$= -(3t^2)(2t) = -6t^3$$

at  $t = 1$  s

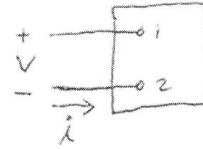
$P = -6$  W so the device is supplying power




$$B) W = \int_0^1 P dt = \int_0^1 -6t^3 dt = -\left. \frac{6t^4}{4} \right|_0^1 = -1.5 \text{ J}$$

so it supplies energy


2) a) Find the current I

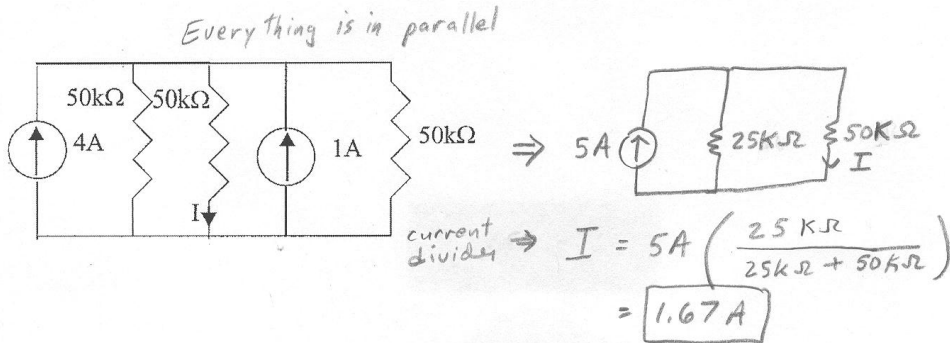

b) Find the voltage V

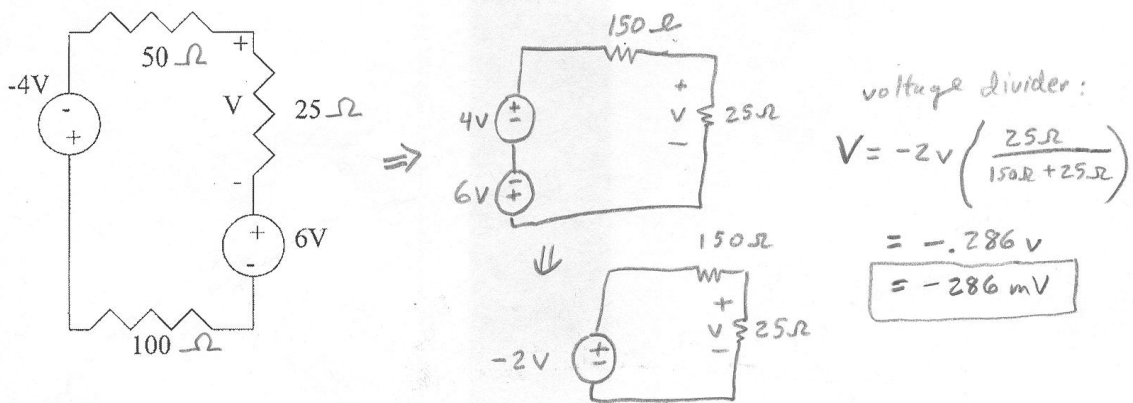

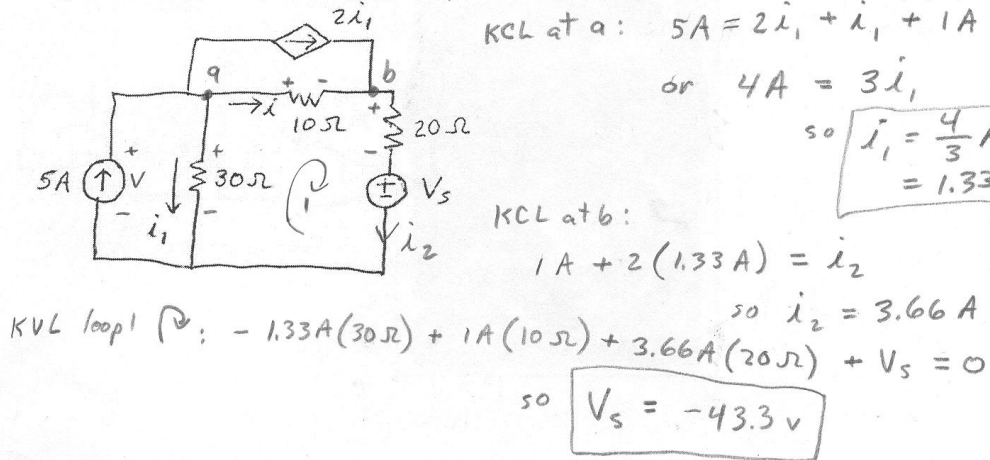3) If  $i = 1A$ , find  $i_1$  and  $V_s$  and do a power check. (There is room on the next page.)



power check:

since it's in parallel with  $\rightarrow$

$$P_{5A} = -(5A)V = -(5A)(1.33A)(30\Omega) = -199.5W$$

$$P_{30\Omega} = i_1^2(30\Omega) = 53.067W$$

$$P_{10\Omega} = i^2(10\Omega) = 10W$$

$$P_{20\Omega} = i_2^2(20\Omega) = (3.66A)^2(20\Omega) = 267.912W$$

$$P_{V_s} = (3.66A)(-43.3V) = -158.48W$$



$$P_{\diamond} = 2(1.33A)(10V) = 26.6W$$

$$\sum P_{\text{used}} = 357.6W$$

$$|\sum P_{\text{supplied}}| = 357.9W$$

so yes  
these are  
 $\approx$  equal

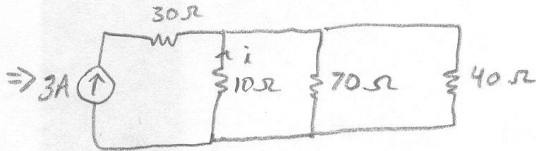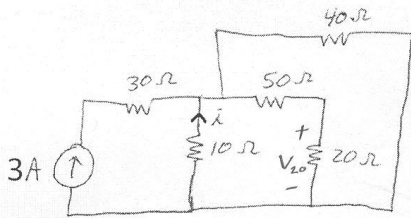- 4) Find the equivalent resistance of the circuit shown as seen by the current source and also find the current  $i$  and the voltage across the  $20\Omega$  resistor.



so  $R_{eq} = 37.179\Omega$



so  $V = 3A(7.179\Omega) = 21.537V$

this is the volts across the  $10\Omega$  resistor since it is in parallel. So,

$$i = -\frac{21.537V}{10\Omega} = -2.1537A$$

$-2.15A$

assuming  $V_{20}$  is defined as shown in the original circuit,

$$V_{70} = V = 21.537V$$



then voltage divider:

$$V_{20} = 21.537V \left( \frac{20\Omega}{20\Omega + 50\Omega} \right)$$

$6.15V$

5) A D'Arsonval movement is rated at 10 mV, 100  $\mu$ A. It is to be used to make a voltmeter whose full scale reading is 125 volts.

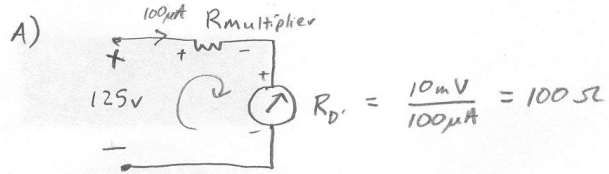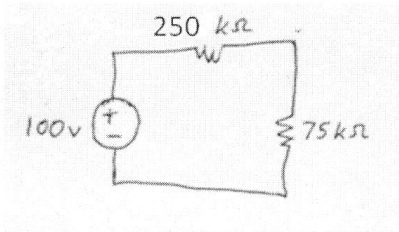
- A) What is the multiplier resistor that must be added in order to make this voltmeter?  
 B) What is the total resistance of this voltmeter?  
 C) If it is to be used to measure the voltage across the 250 k $\Omega$  resistor in the circuit shown, what would this voltmeter read?  
 D) What would an ideal voltmeter read for the voltage across the 250 k $\Omega$  resistor?



KVL:  $-125 \text{ V} + 100 \mu\text{A} (R_{\text{multiplier}}) + 10 \text{ mV} = 0$

so  $R_{\text{multiplier}} = 1,249,900 \Omega = 1.2499 \text{ M}\Omega$

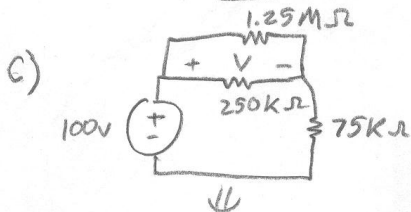B)  $R_{\text{meter}} = R_{\text{multiplier}} + R_D$   
 $= 1,250,000 \Omega$   
 $= 1.25 \text{ M}\Omega$



need to find  $V$ .


$\Downarrow$

$\Rightarrow$  voltage divider  $\Rightarrow V = 100 \text{ V} \left( \frac{208.3 \text{ k}\Omega}{208.3 \text{ k}\Omega + 75 \text{ k}\Omega} \right) = 73.5 \text{ V}$

D) Ideal voltmeter has  $R = \infty$

so  $\Rightarrow V = 100 \text{ V} \left( \frac{250 \text{ k}\Omega}{250 \text{ k}\Omega + 75 \text{ k}\Omega} \right) = 76.9 \text{ V}$

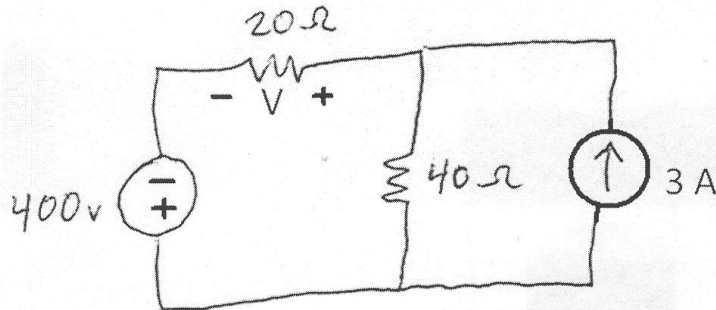
- 6) Use Orcad Pspice for the circuit below to find the voltage V. Be sure to printout your results and be sure your name is typed on the printout and indicate your answer on your printout or in the space below. If you can't get Pspice to run, at least print out your circuit.



$$V = 173,3\text{v}$$

see printout.

5	4	3	2
---	---	---	---

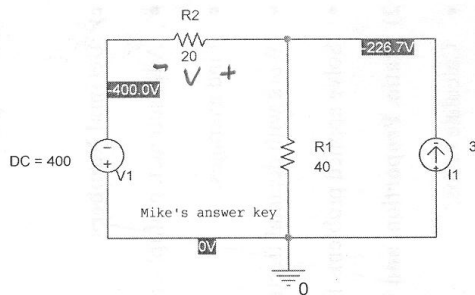

the question wants V (shown above).

$$V = 173.3\text{v}$$

$$= (-226,7 - (-400\text{v}))$$