
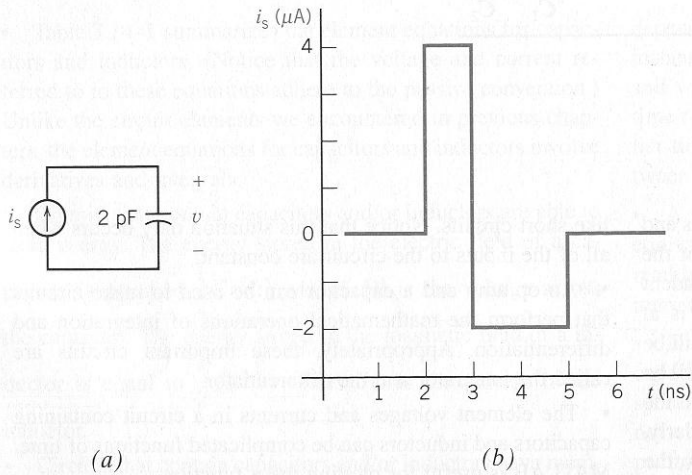


ENGR&204 Spring 2011 Homework #5 Due in one week.

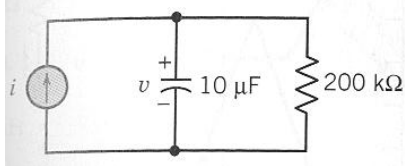Find $v(t)$ when $v_o(0^-) = -1.0 \text{ mV}$.




Calculate i if $v = 5(1 - 2e^{-2t}) \text{ V}$




A capacitor is used in a camera electronic flash. A small battery with a constant voltage of 6.0 v is used to charge the capacitor with a constant current of 10 μA . How much time does it take to charge the capacitor when $C = 10 \mu\text{F}$? What is the stored energy?

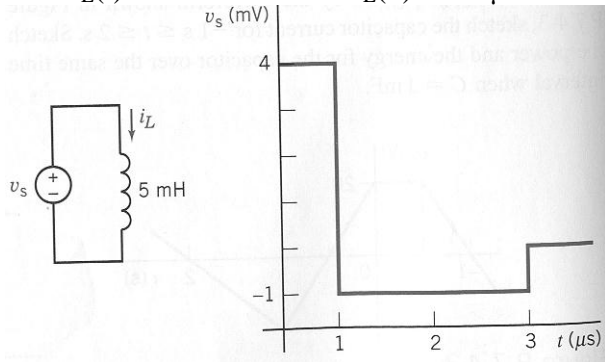Find $i_L(t)$ when $t > 0$ when $i_L(0) = -2 \mu\text{A}$.



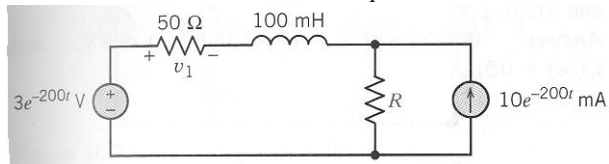What is R for the circuit if $v_1 = e^{-200t} \text{ V}$ for $t \geq 0$?



The switch has been opened for a long time before closing at $t = 0 \text{ s}$. What is $v_c(0^+)$ and $i_L(0^+)$, the values of the capacitor voltage and inductor current immediately after the switch is closed? Find $v_c(\infty)$ and $i_L(\infty)$, the values of the capacitor voltage and inductor current after the switch has been closed for a long while.

