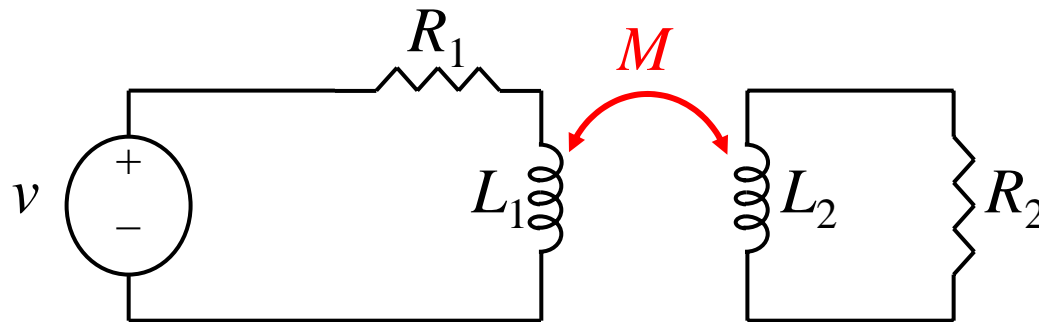


Lecture 14

- **Mutual Inductance**
 - **Chapter 6.4-6.5**

Mutual Inductance

- Def: Inductance is the circuit parameter that relates a voltage to a time-varying current in the same circuit (“self-inductance”).
- If a magnetic field links two circuits then we obtain mutual inductance (in addition to self-inductance).



$$L_1 \frac{di_1}{dt}$$

$$+ M \frac{di_2}{dt}$$


$$L_2 \frac{di_2}{dt}$$

$$+ M \frac{di_1}{dt}$$

self-inductance


mutual inductance

Dot Convention

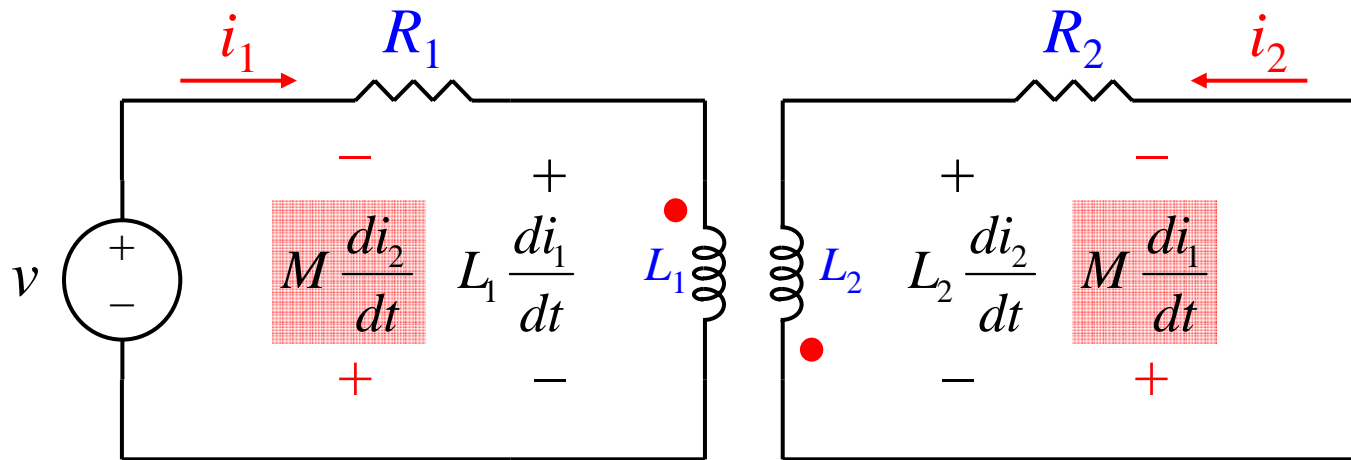

- When the reference direction for a current enters the dotted terminal of a coil, the reference polarity of the voltage that it induces in the other coil is positive at its dotted terminal.
- $-v + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0$
- $i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0$

Example

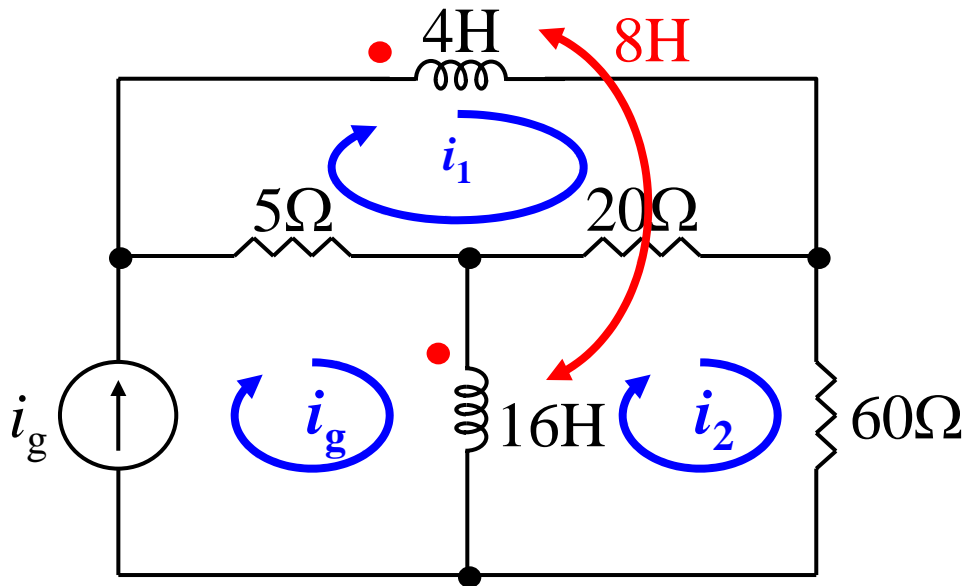


- Mesh current method:

$$4di_1/dt + 8d(i_g - i_2)/dt + 20(i_1 - i_2) + 5(i_1 - i_g) = 0$$

$$20(i_2 - i_1) + 60i_2 + 16d(i_2 - i_g)/dt - 8di_1/dt = 0$$

- If $i_g = 16\text{A}$ after steady state is reached, then how much energy is stored in this circuit?

Example (in steady state)

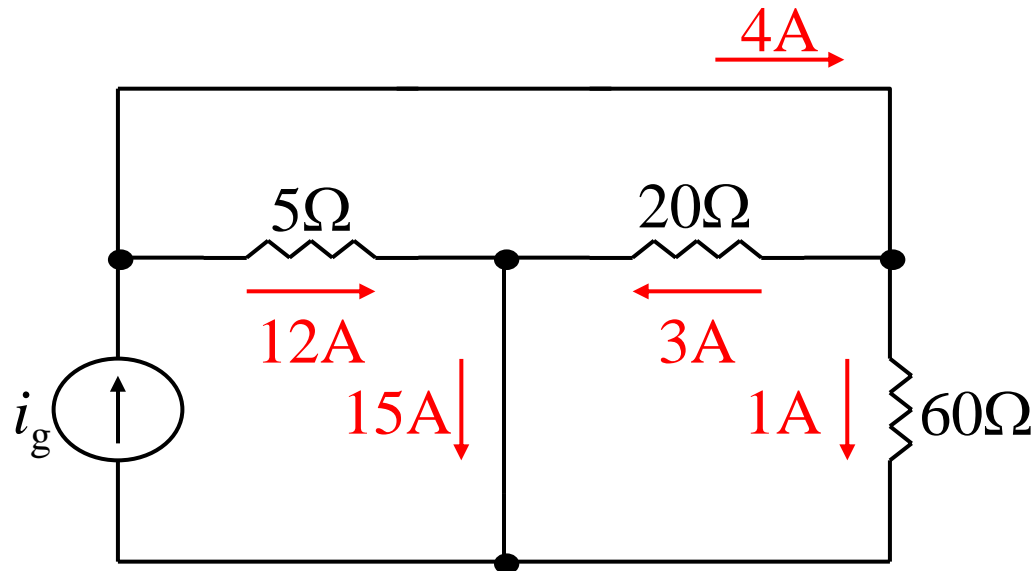

- Determine mesh currents:
 - If all mesh currents are constant, then inductors behave like short circuits.
- $1/R_{eq} = 1/5 + 1/20 + 1/60 = 16/60 = 4/15 \Omega^{-1}$
- $i_g = 16\text{A}$, $v_g = 60\text{V}$, $i_2 = 1\text{A}$, $i_1 = 4\text{A}$
- $W = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 (i_g - i_2)^2 + M i_1 (i_g - i_2)$
 $= \frac{1}{2} 4 16 + \frac{1}{2} 16 15^2 + 8 4 15 = 32 + 5000 + 480 = 5512\text{J}$


Coupling Coefficient

- It can be shown that $M^2 = k^2 L_1 L_2$ for a constant k with $0 \leq k \leq 1$.
- k depends on the physical arrangement of the inductors.
 - $k = 0$ no coupling
 - $k = 1$ ideal coupling



Energy and Mutual Inductance (1)

- Generic Example:

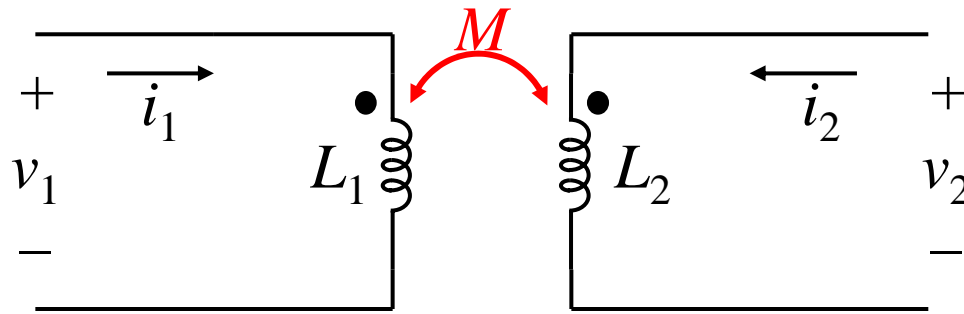

– Assume that initially, $i_1 = 0$ and $i_2 = 0$.


– Then gradually increase i_1 to I_1 :

$$w_1 = \int_0^{W_1} dw = L_1 \int_0^{I_1} idi = \frac{1}{2} L_1 I_1^2$$

– Then gradually increase i_2 to I_2 :

$$w_2 = \int_{W_1}^{W_2} dw = M \int_0^{I_2} I_1 di + L_2 \int_0^{I_2} idi = I_1 I_2 M + \frac{1}{2} L_2 I_2^2$$

Energy and Mutual Inductance (2)

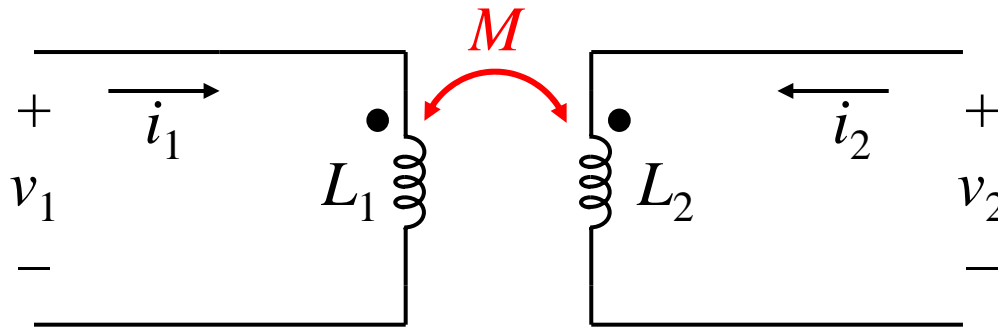

sign depends
on dots

- Total energy:

$$w = w_1 + w_2 = \frac{1}{2} L_1 I_1^2 + M I_1 I_2 + \frac{1}{2} L_2 I_2^2$$

- This equation holds in general, for any point in time:

$$w = \frac{1}{2} L_1 i_1^2 \pm M i_1 i_2 + \frac{1}{2} L_2 i_2^2$$

- Note that because of $M = k\sqrt{L_1 L_2}$ with $0 \leq k \leq 1$ w is always non-negative.