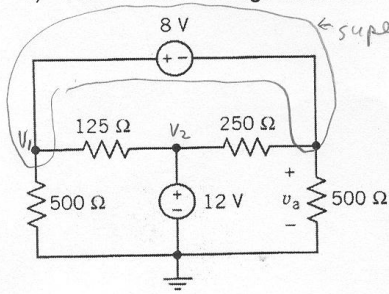


Show work. Use a different method than asked and you lose at least 5 points.

1) Use the node voltage method to find v_a .



$v_2 = 12\text{ v}$


KCL supernode: $\frac{v_1}{500} + \frac{v_1 - 12}{125} + \frac{v_a - 12}{250} + \frac{v_a}{500} = 0$

also $v_1 - v_a = 8$

solved with Matlab

$v_1 = 12\text{ v}$
 $v_a = 4\text{ v}$

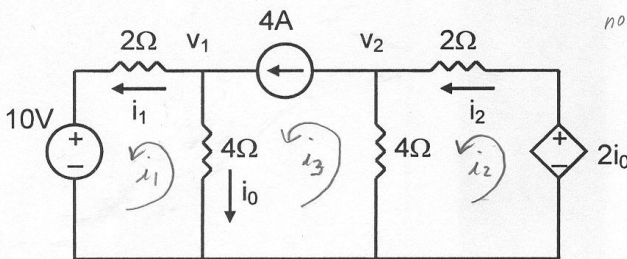2) Using the mesh-current method, find i_1 , i_2 , and v_1 .



note: $i_3 = 4\text{ A}$

KVL mesh 1: $10 + 4(i_1 - i_3) + 2i_1 = 0 \Rightarrow 10 + 4i_1 - 16 + 2i_1 = 0$
 $6i_1 = 6 \Rightarrow i_1 = 1\text{ A}$

KVL mesh 3: $v_2 - v_1 + 4(i_3 - i_1) + 4(i_3 - i_2) = 0$
 or $v_2 - v_1 + 4(4 - 1) + 4(4 - i_2) = 0$
 or $v_2 - v_1 + 12 + 16 - 4i_2 = 0$
 or $v_2 - v_1 + 28 - 4i_2 = 0$


don't need this!

KVL mesh 2: $-2i_0 + 2i_2 + 4(i_2 - i_3) = 0$ but $i_0 = \frac{v_1}{4}$
 or $-2(3) + 2i_2 + 4i_2 - 16 = 0$ and $v_1 = 10 + 2i_1$


or $6i_2 = 22 \Rightarrow i_2 = 3.67\text{ A}$ so $i_0 = \frac{10 + 2i_1}{4}$

and $v_1 = 10 + 2i_1 = 10 + 2(1) = 12\text{ V}$
 $= \frac{10 + 2}{4} = 3\text{ A}$

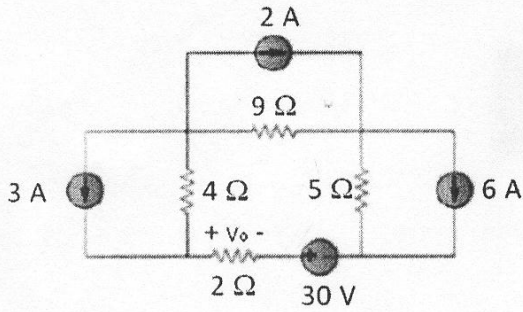
3) Find v_o in the circuit below using source transformations.



$\Rightarrow 12$

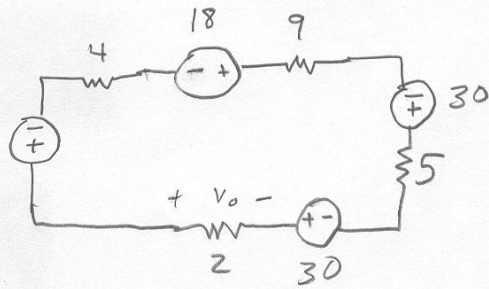

\Downarrow

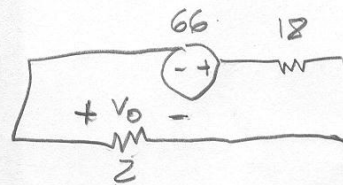


so

$$v_o = -66 \left(\frac{2}{2+18} \right)$$

$$= \boxed{-6.6 \text{ V}}$$

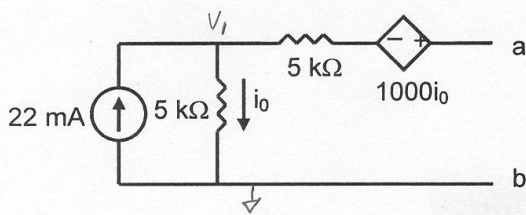
- 4) A) Find the Thévenin equivalent circuit at terminals a – b.
 B) What is the maximum power that can be delivered to a resistor attached across terminals a – b?



method 2A find $V_{ab} = V_{oc} = V_{th}$
 $V_1 = (5k)(22m) = 110\text{ v}$
 and $i_0 = 22\text{ mA}$

so $V_{oc} = V_1 + 1000i_0$ (since no current thru 5k, no volts lost there)
 $= 110 + 1000(22m)$
 $= 132\text{ v}$
 $= V_{th}$

method 2B:
 now add a short;

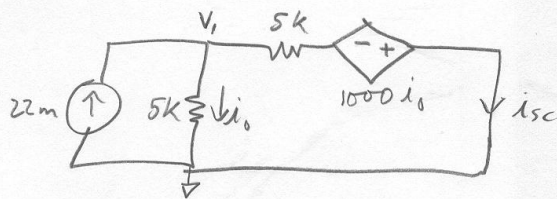

In terms of node voltage V_1 node 1:
 $i_{sc} = \frac{V_1 + 1000i_0}{5k}$

and $V_1 = i_0(5k)$ sub in

so $i_{sc} = \frac{V_1 + 1000\left(\frac{V_1}{5000}\right)}{5000}$
 $= \frac{V_1 + \frac{V_1}{5}}{5000}$
 $= \frac{V_1}{5k} + \frac{V_1}{25k}$
 $= \frac{1.2V_1}{5k}$

now
 KCL node 1: $-22m + \frac{V_1}{5k} + i_{sc} = 0$

$-22m + \frac{V_1}{5k} + \frac{1.2V_1}{5k} = 0$


solve; $V_1 = 50\text{ v}$

so $i_{sc} = \frac{1.2V_1}{5k} = \frac{1.2(50)}{5k}$


$= 12\text{ mA}$

so $R_{th} = \frac{V_{th}}{i_{sc}} = \frac{132\text{ v}}{12\text{ mA}} = 11\text{ k}\Omega$

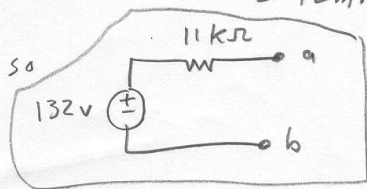
b.) $P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(132\text{ v})^2}{4(11k\Omega)} = 396\text{ W}$
 $= 396\text{ mW}$



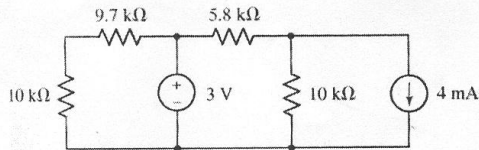
5) Use superposition to find the current through the 5.8kΩ resistor.



turn off 4mA source:

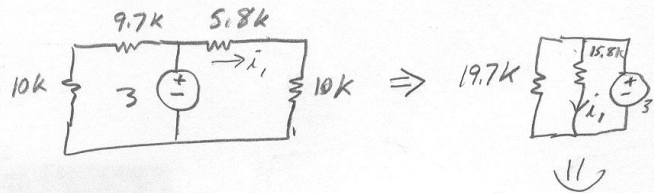

turn off 3V source:

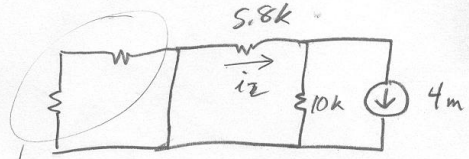

Shorted out so ignore

current divider

$$i_2 = 4m \left(\frac{10k}{10k + 5.8k} \right)$$

$$= 2.53 \text{ mA}$$

so

$$i = 2.72 \text{ mA} \rightarrow$$


Ohm's law

$$i_1 = \frac{3V}{15.8k}$$

$$= 190 \mu A$$

6) A) Find v_o in terms of v_s .

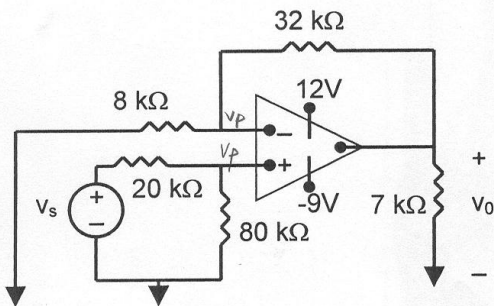B) Find the range of values for v_s such that the op amp remains in its range of linear operation.



voltage divider: $V_p = V_s \left(\frac{80k}{80k + 20k} \right) = V_s (0.8)$

KCL at - input:

$$\frac{V_s (0.8) - 0}{8k} + \frac{V_s (0.8) - V_o}{32k} = 0$$

$$\frac{3.2V_s + 0.8V_s - V_o}{32k} = 0$$

so

$$V_o = 4V_s$$

when $V_o = 12v$, $V_s = \frac{12}{4} v = 3v$

when $V_o = -9v$, $V_s = \frac{-9}{4} v = -2.25v$

so

$$-2.25v \leq V_s \leq 3v \text{ to be in linear range}$$